

LAB2-MC

Sensors and DC Motors

CMP(N)211

Spring 2021

By: Salma Abdel Monem

Lab Objectives

- ✓ Control DC motors using PWM and H-bridge
- ✓ Read Analog Signals.
- ✓ Pull up resistance.
- ✓ Temperature sensors types
- ✓ Map thermistor readings to Celsius temperature
- ✓ Use the SimuLIDE.

Recap

Till Now we have learnt the following:



- ✓ Read Digital Signals . Example ?
- ✓ Write Digital Signals. Example ?

Now it's time to learn how to Read and Write Analog Signals


PWM

We will get into it's details in the next lab.

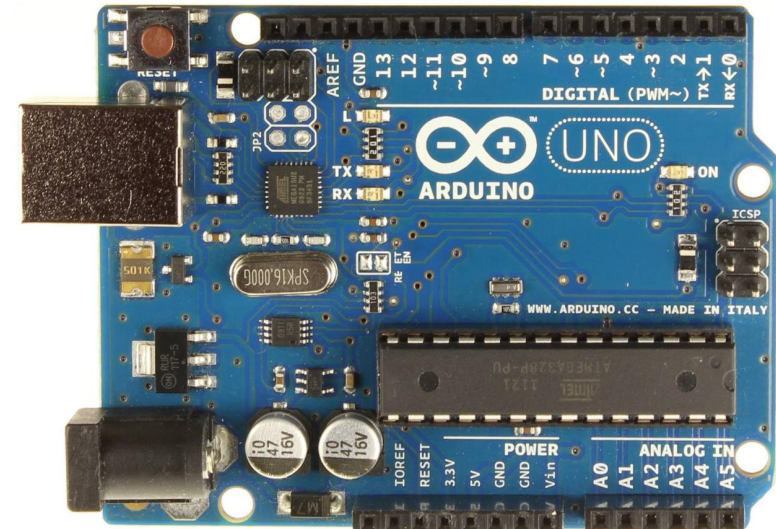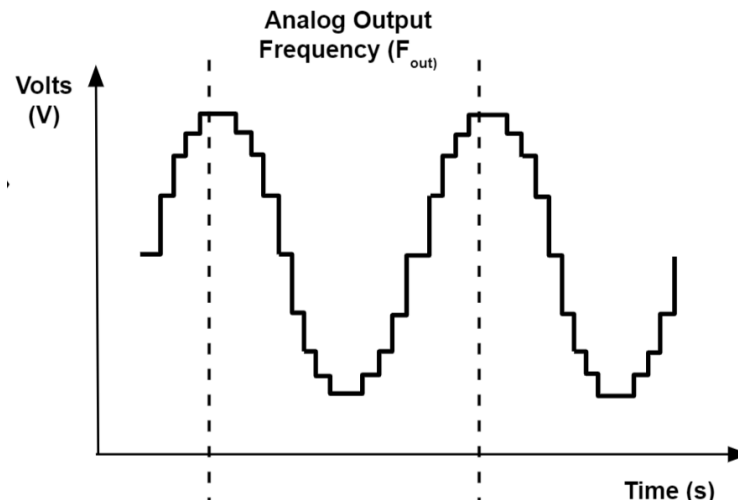- ✓ Till now, what you need to know is that PWM pins(~) produce Analog like / discretized signal from (0 to 255).
- ✓ Example of writing to PWM pin `analogWrite(9, 255);`




DC motors

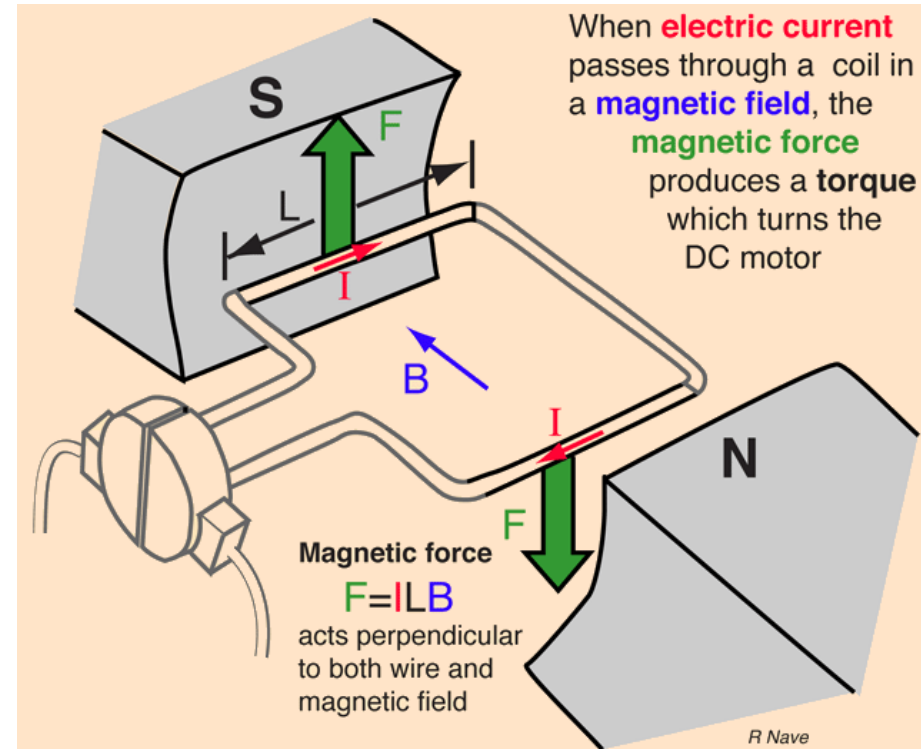


DC motors and H-Bridge

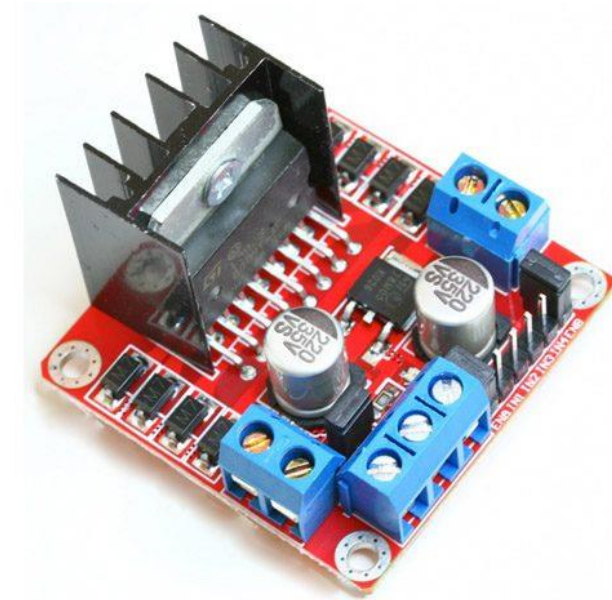- ✓ The H-Bridge (L298p here) can be used to control the direction of the spinning of the motor and it's speed as well.





DC motors and H-Bridge

✓ L298p can connect two motors

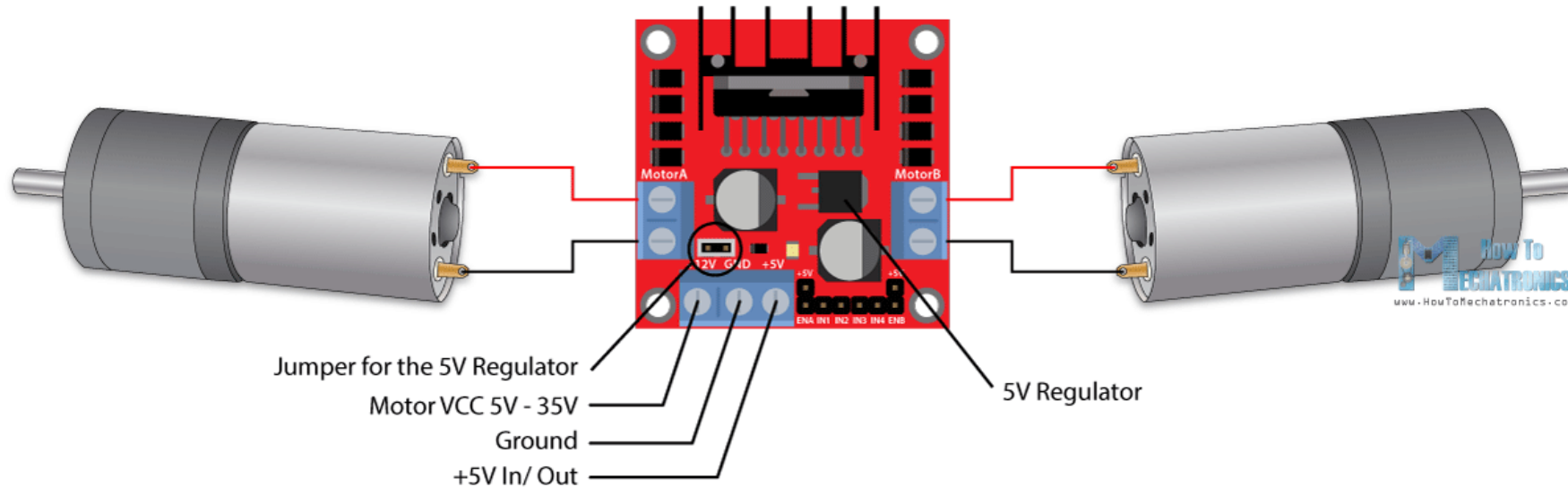

DC motors and H-Bridge


✓ L298p pinout

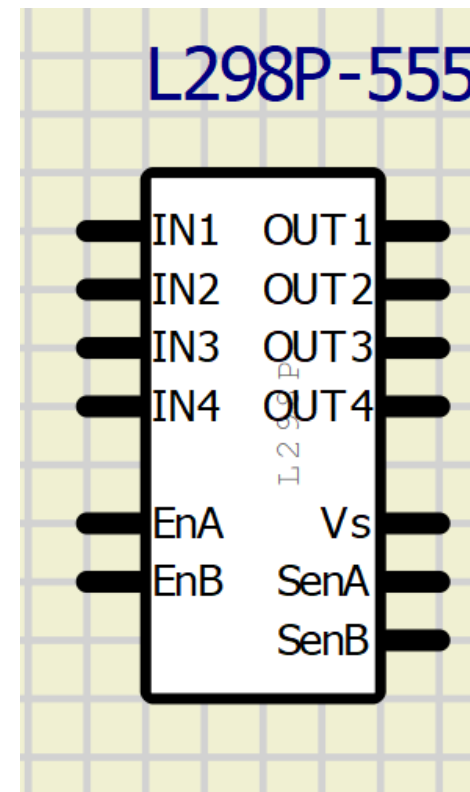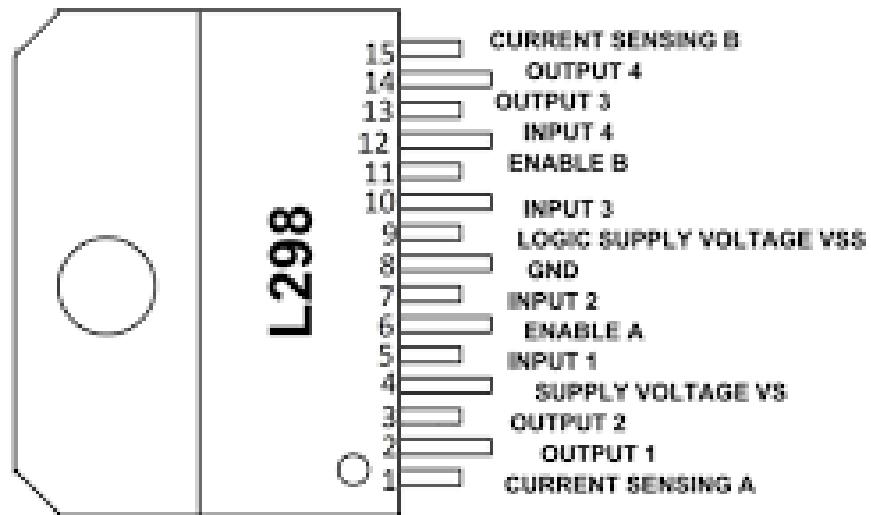

DC motors and H-Bridge

L298p Pinout

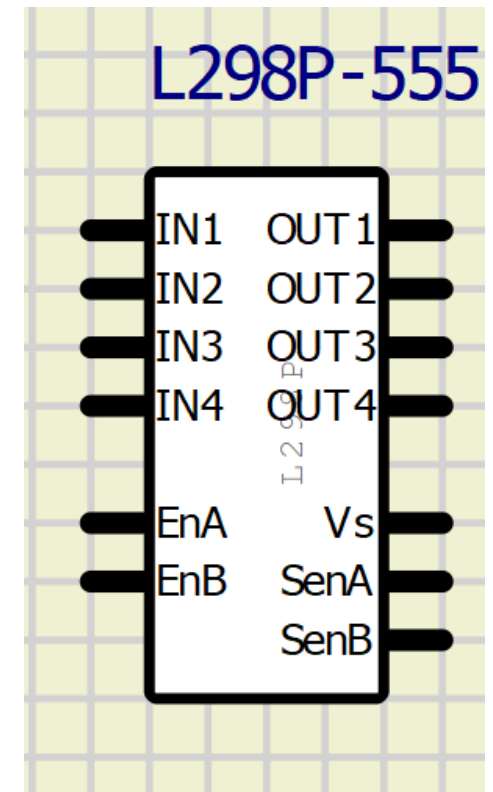
- ✓ IN1 and IN2 control direction of motor 1 (arduino)
- ✓ IN3 and IN3 control direction of motor 2 (arduino)
- ✓ EnA controls the speed of the motor 1 (PWM arduino)
- ✓ EnB controls the speed of the motor 2 (PWM arduino)
- ✓ OUT1 and OUT2 are connected to the both edges of the motor 1
- ✓ OUT3 and OUT4 are connected to the both edges of the motor 2
- ✓ Vs is connected to 3.3 v from arduino



DC motors and H-Bridge


L298p Pinout

IN1	IN2	MOTOR
0	0	BRAKE
1	0	FORWARD
0	1	BACKWARD
1	1	BRAKE

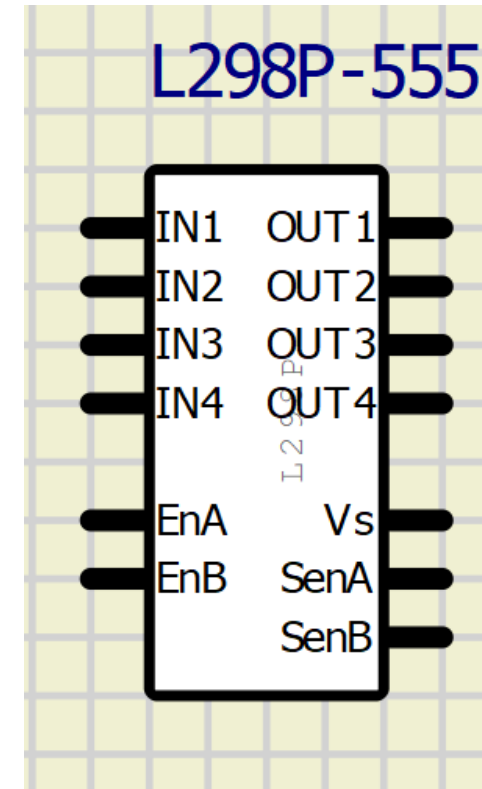


Read Analog Signal

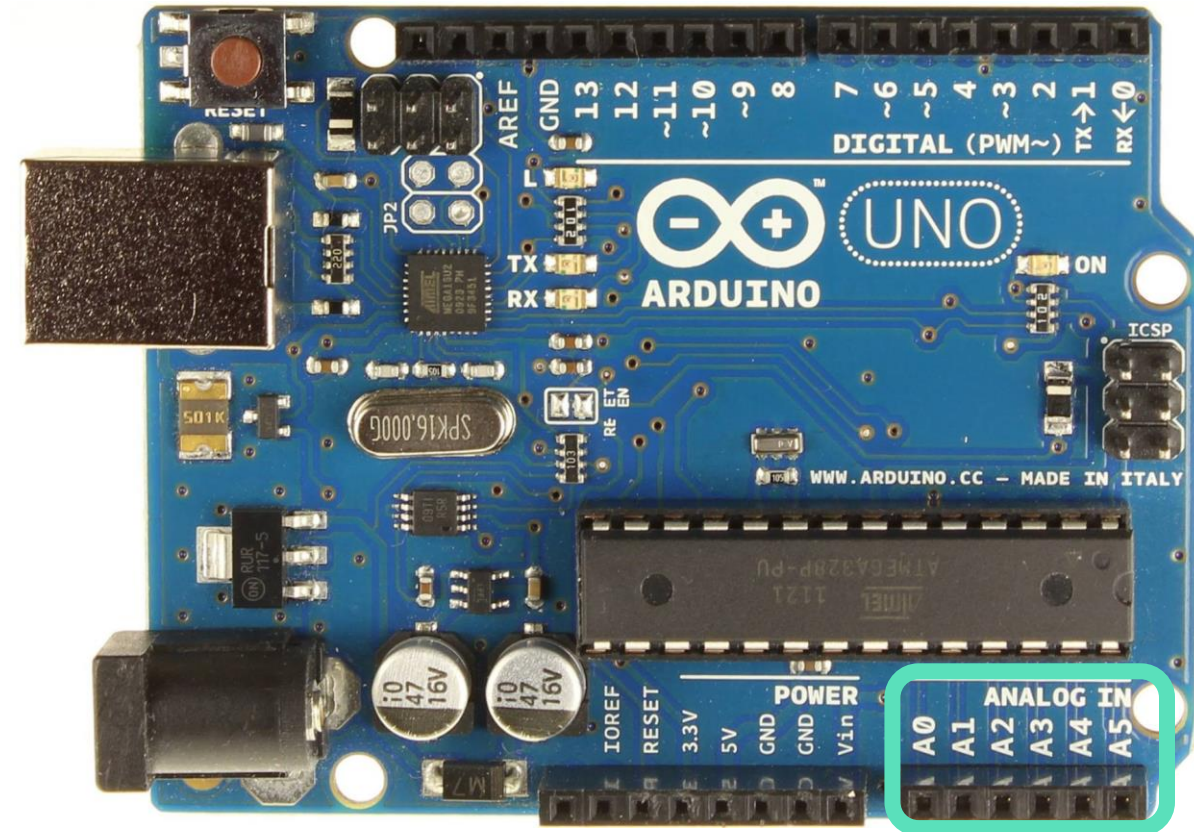- Use the analog pins {A0A5} to read analog signals.
- The analog input can vary from { 0 to 1023} .
- You might want to map 0 to LOW , and 1023 to HIGH {5volt} in Arduino.
- Pin numbers are (0 : 5) and no need to set them as inputs in the setups.
- Use `analogRead(Pin)`




Temperature sensor types

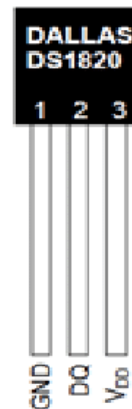- Thermistor (cheap , wide range , less accurate, non linear)
- Thermocouple
- RTDs (resistive temperature detectors)
- Digital thermometer Ics (more expensive, more accurate, linear)
- Analog thermometer ICs



Digital thermometer Ic sensor (DS1820)



- It has three legs like the following:

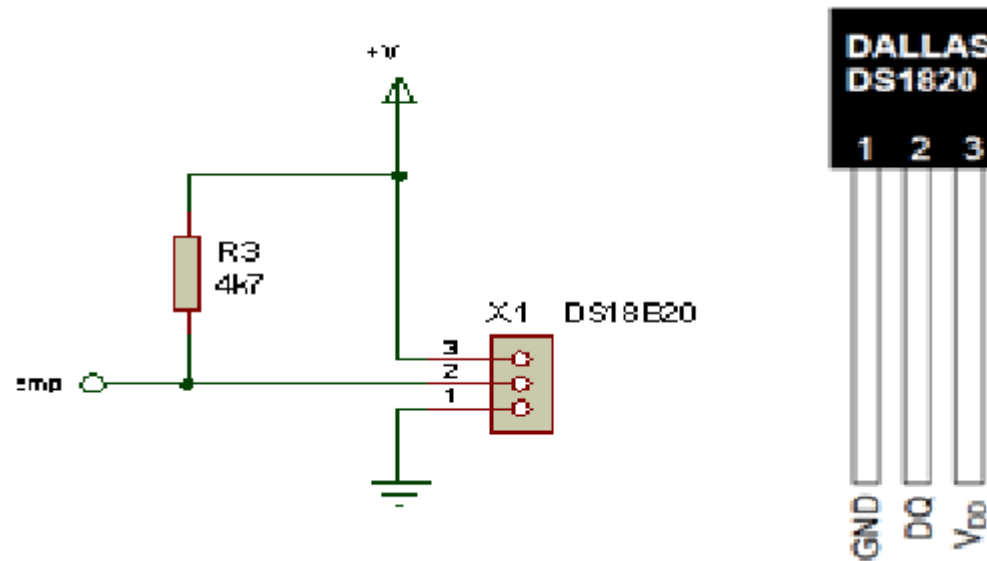

So let's connect it with an Arduino ??

Yet this is not recommended !



Pretty Easy right?

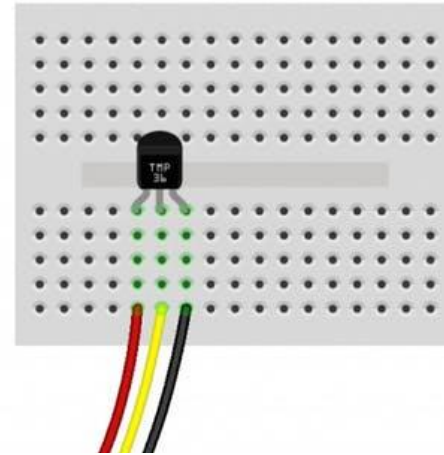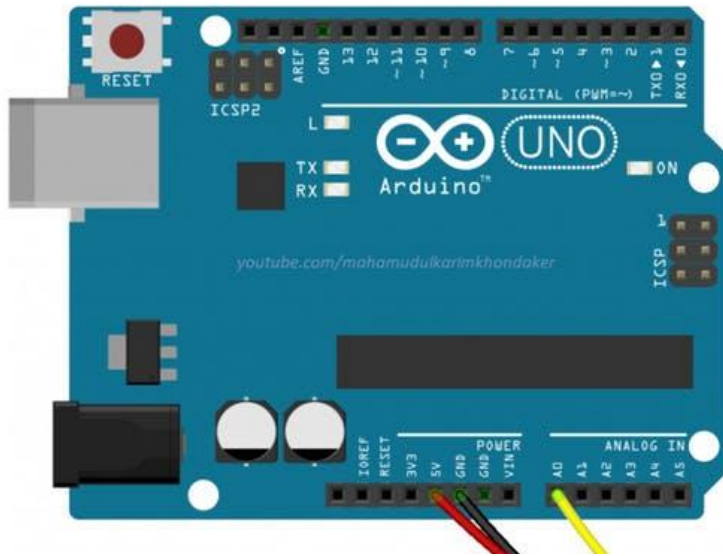

This might cause unstable readings if the sensor is not sending a reading signal



Solution? Pull Up resistors

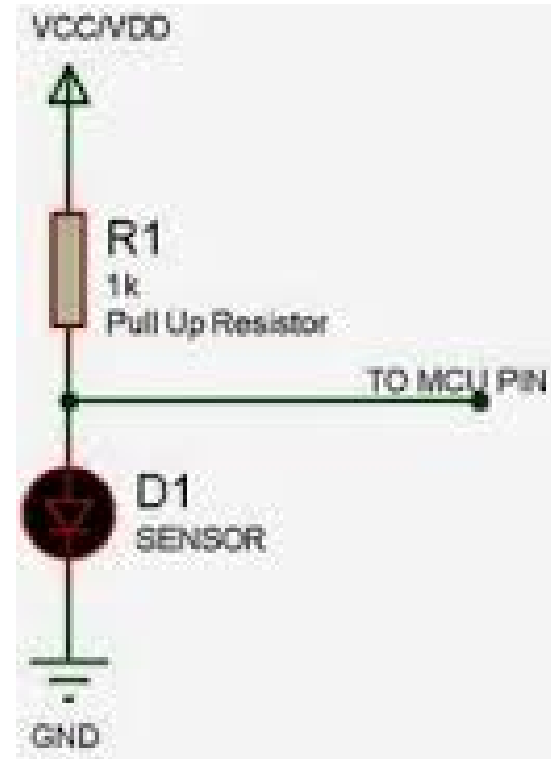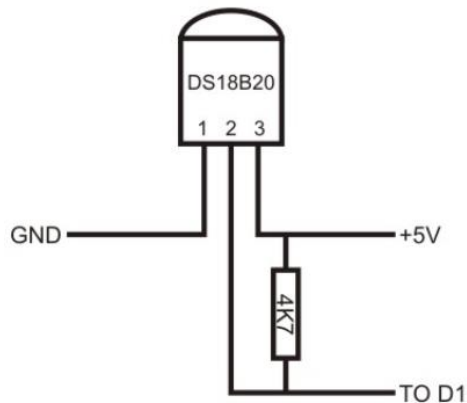- What happens when the sensor is open circuit?
- Answer is : floating input !!




Solution? Pull Up resistors

- The sensor is open circuit

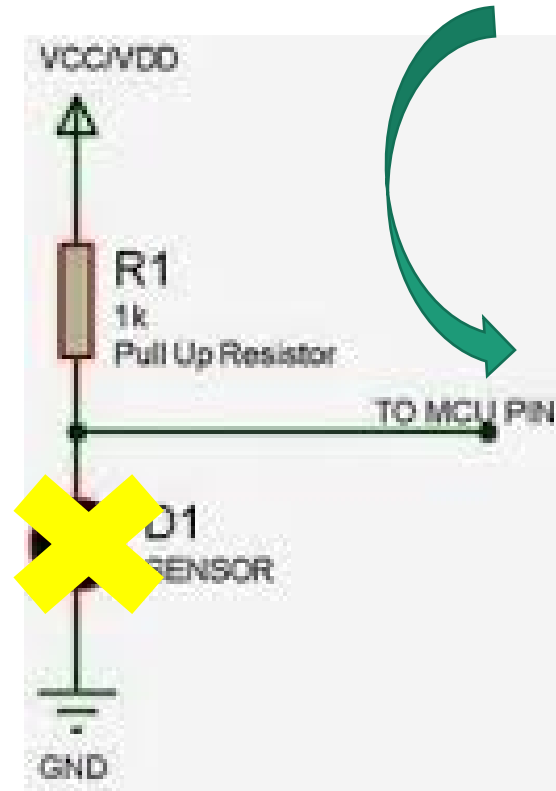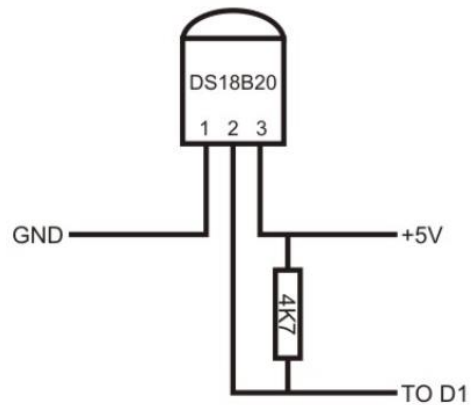


Solution? Pull Up resistors

- The sensor is closed circuit

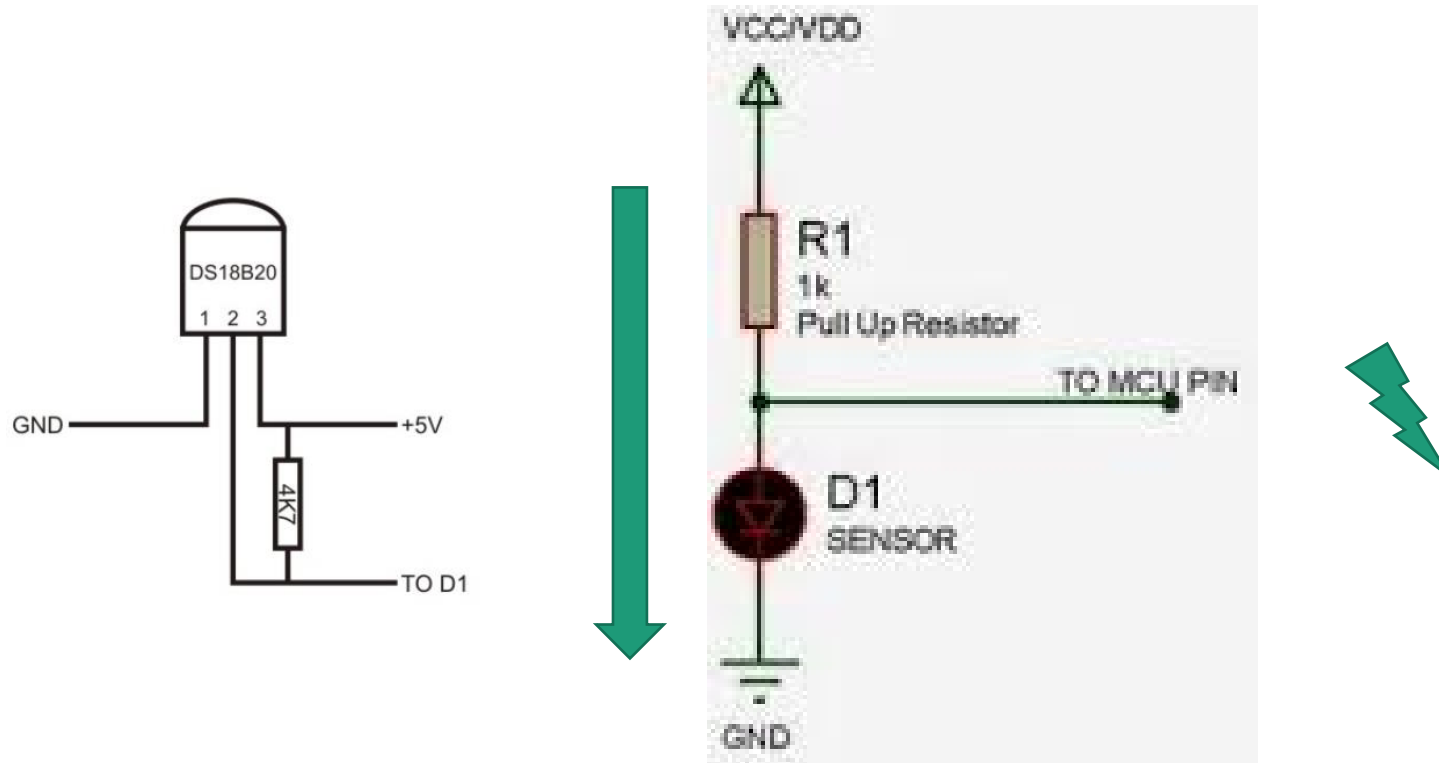

What will be the reading then?


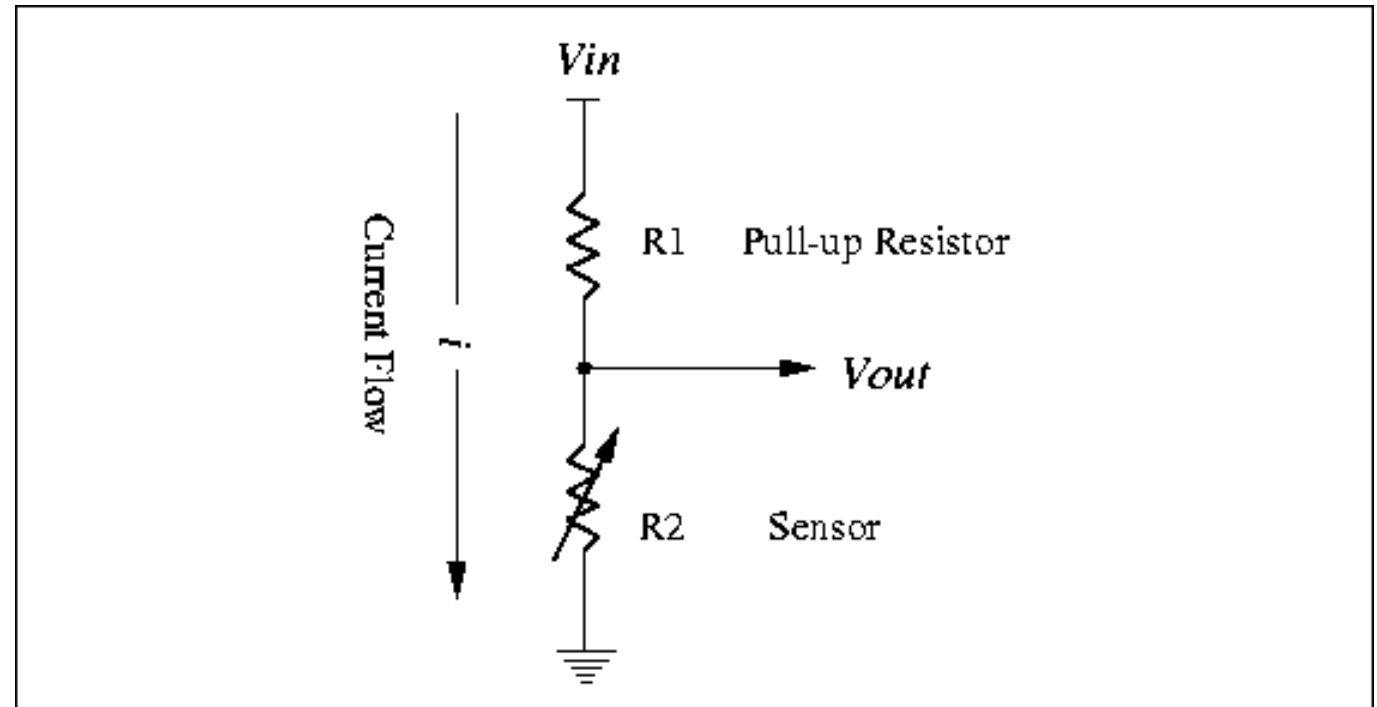
- Remember the voltage divider rule.
- When the sensor is closed-circuit; it's resistance changes with the temperature.
- The reading voltage V_{out} is then what the Arduino senses.



$$V_{out} = \frac{R2}{R1 + R2} * V_{in}$$



Then how should we connect it ?

- Using a pull-up resistance

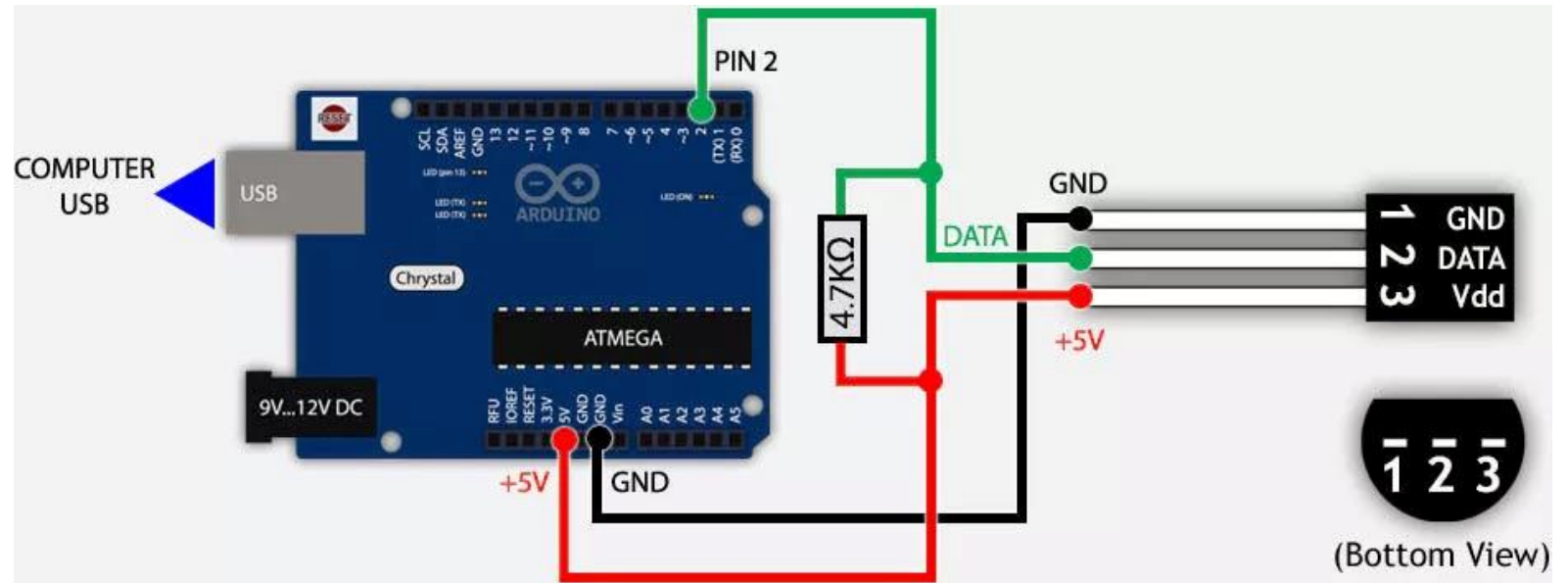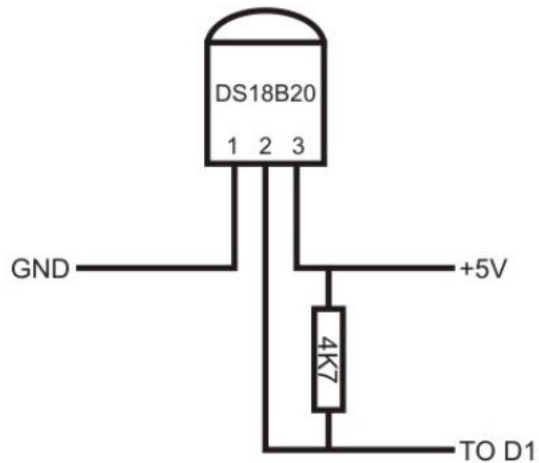

Then how should we connect it ?

- Using a pull-up resistance

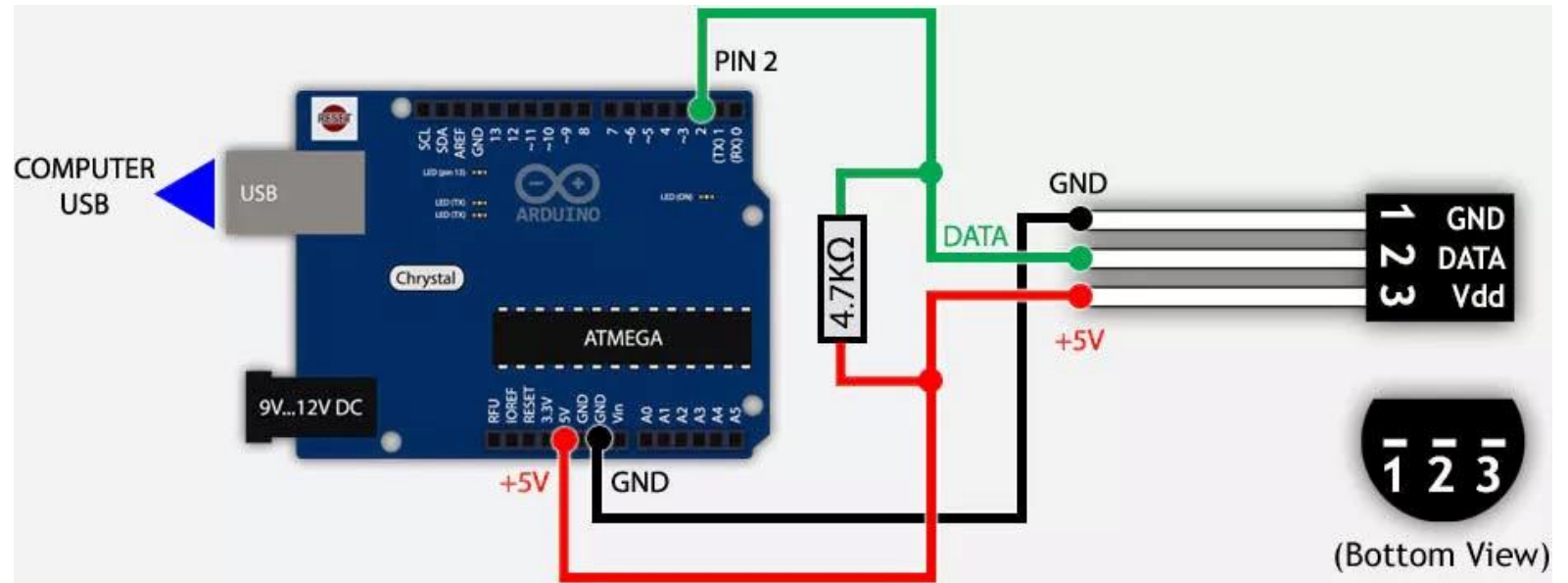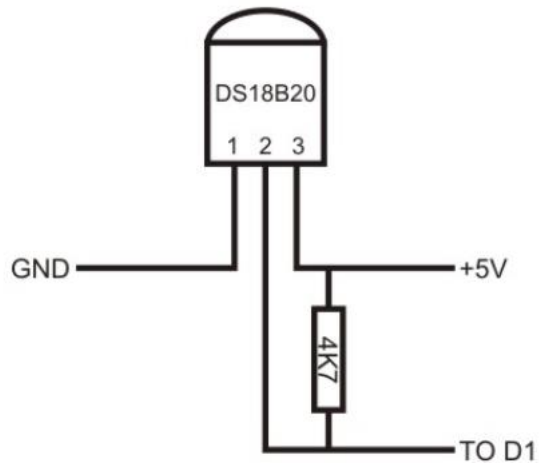


Additional notes

- You have first to use the 1-wire library with arduino.
- Following the steps in this [site](#).
- You can also see the details of the ADC in the [datasheet](#).
- It has linear mapping between the reading and the temperature.



Thermistor(NTC)

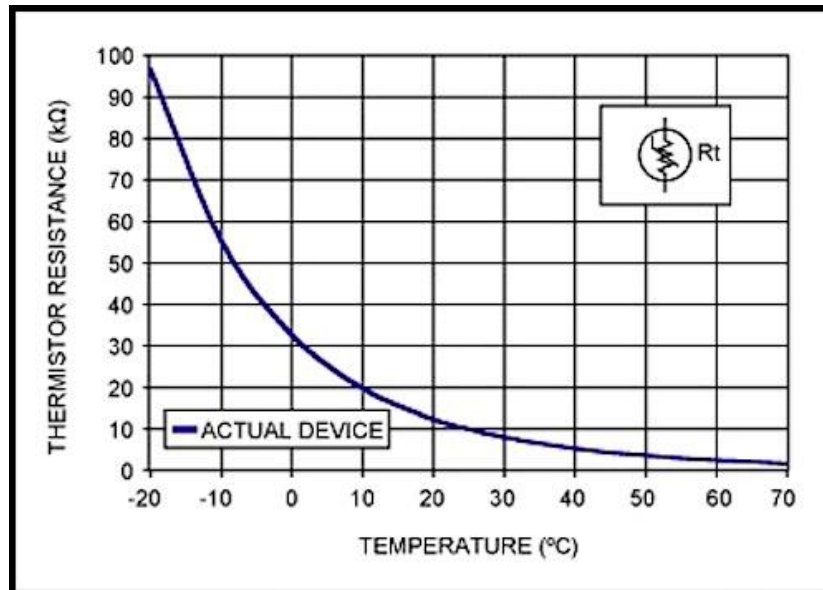- It has two legs like the following
- Simple and cheap but it doesn't have linear mapping for temperature vs. it's analog readings.





Thermistor(NTC)

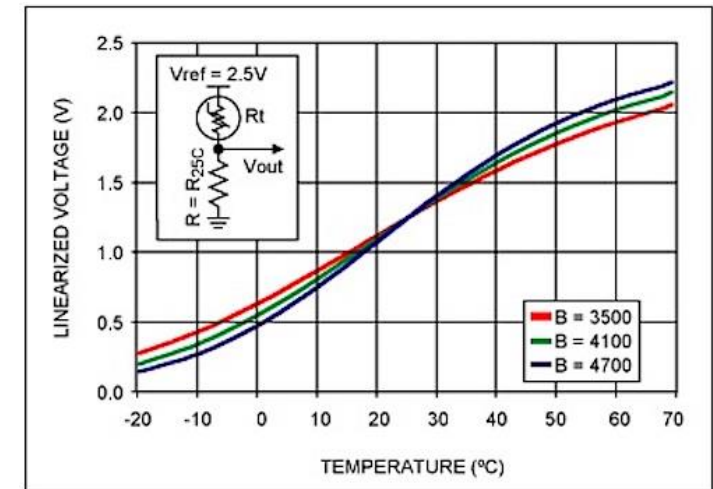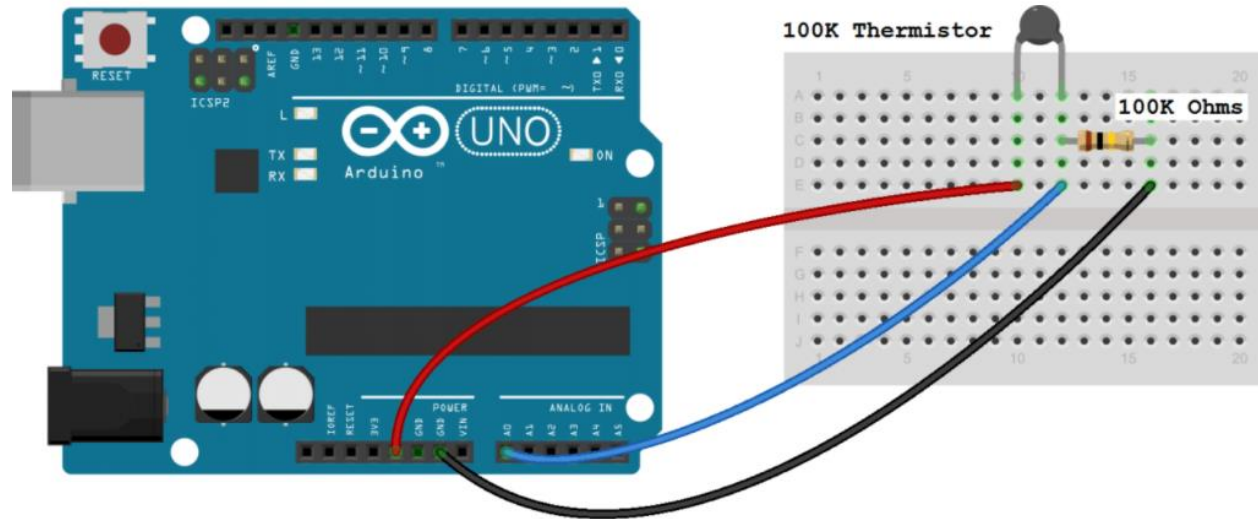- Linear mapping technique ([Voltage Mode Linearization](#))
- Places the thermistor in series with a normal resistor forming a voltage divider circuit.



Thermistor(NTC)

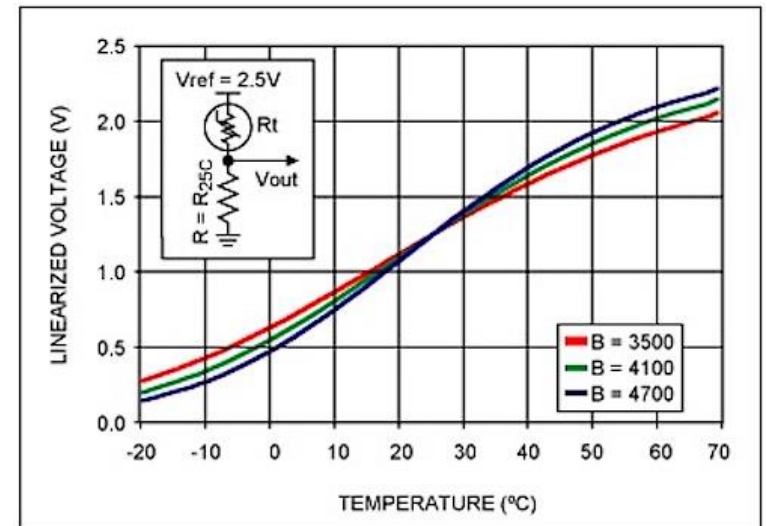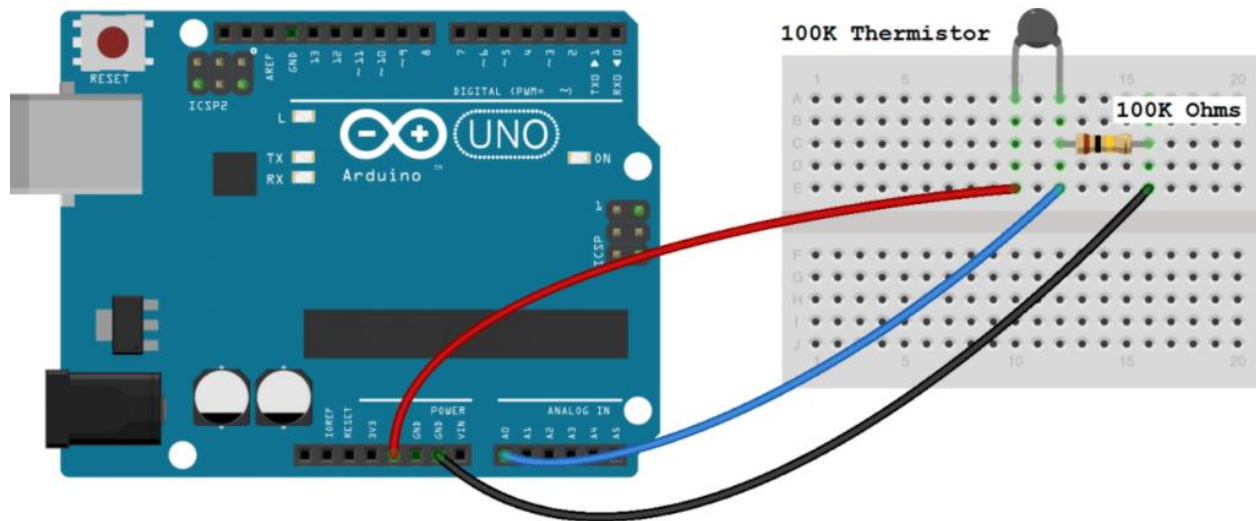- Linear mapping technique ([Voltage Mode Linearization](#))
- If the resistor's value is equal to the thermistor's resistance at room temperature, then the region of linearization will be symmetrical around room temperature




So what is the actual temperature ?

- Remember that the Arduino reads the voltage V_{out} .
- Using the voltage $V_{in}=1023$ and V_{out} (reading) from $\{0:1023\}$ we can get the sensor's resistance right ?

$$V_{out} = \frac{R1}{R1 + R2} * V_{in}$$


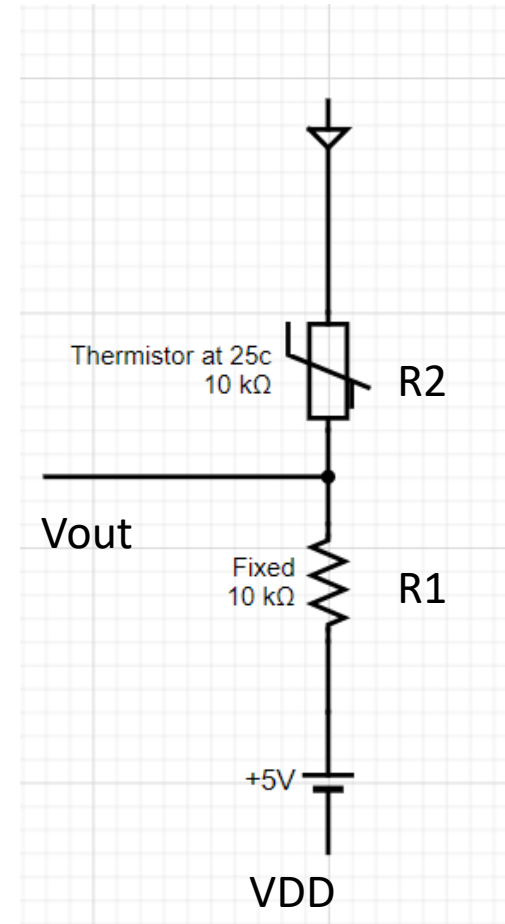
$$R2 = R1 / \left(\frac{V_{in}}{V_{out}} - 1 \right)$$




So what is the actual temperature ?

$$R2 = R1 / \left(\frac{V_{in}}{V_{out}} - 1 \right)$$

- Using the “Steinhart–Hart equation”
- A,B and C are constants related with the sensor.
- T is temperature and R is the sensor’s resistance.

$$\frac{1}{T} = A + B \ln R + C(\ln R)^3,$$

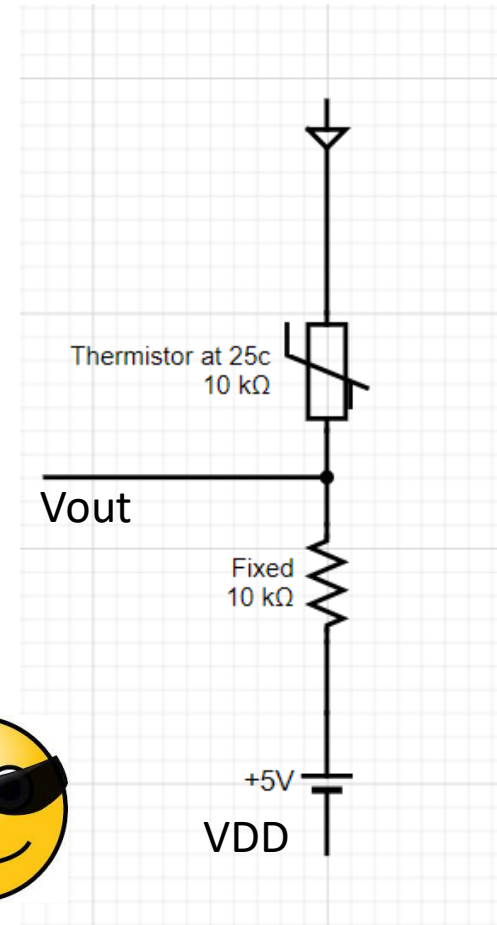- T is the current temperature + 273.15 (To at 25 C)
- So subtract 273.15 from T and you got the temperature.



Exercise

- Use the [SimuLIDE](#) to Perform the following requirement.
- Read the temperature from a thermistor and control a dc motor using it.
- If the reading is between (0 and 50 c) the motor stops.
- If the reading is between (51 and 100c) the motor moves forward with half the speed.
- If the reading is higher than 100c the motor moves backwards with maximum speed.
- Submit a link to google drive folder file including your (.ino file , .hex file , .simu file and no more than 3 minutes video showing all the testcases)
- Name all these files with your name _id_lab2.
- No cooperation or plagiarism (individual work).
- Violation of the submission rules will cause zero grade.

Appendix

- Thermistor constants for NTC 10k ohm are :
- float A = 1.009249522e-03, B = 2.378405444e-04, C = 2.019202697e-07;
- You can use log function in arduino instead of ln.